



Trinity College Dublin

Coláiste na Tríonóide, Baile Átha Cliath

The University of Dublin

ASSIGNMENT-2

DIGITAL SYSTEM DESIGN

SUBMITTING TO: SHREEJITH SHANKER

SUBMITTED BY: SHRUTI KATHURIA

Aim:

The purpose of this session is to bring together elements from all your Labs, but particularly Lab F-G, and give you experience with developing and testing a larger sequential design and targeting it to the FPGA board. This assignment is worth 25% of 3C7.

Sequence Detector

You need to design a system that comprises an LFSR, a sequence detecting Finite State Machine (FSM), and a counter, in order to count the number of times a certain codeword (10, 12 bits long) is issued in the stream of bits generated by the LFSR in a full cycle of that LFSR. Each student will be given a different sequence/codeword, found in a separate handout LFSR_code_setup.pdf.

DATA USED IN THE ASSIGNMENT

TCD ID	NAME	BOARD NUMBER	LFSR_WIDTH	SEED VALUE	PATTERN
21355061	KATHURIA SHRUTI	Basys3108	24 xor	100111111001000000000000	11001010000

WORKING OF THE DESIGN:

At first, we made different modules

•Clock:

This helps us to control the speed of the BASYS 3 board. The output of the clock is send to the LFSR module from which we obtain a 24 bit number and max tick indicating that there are $2^{24}-1$ cycles.

•State Machine Module:

In this we drew the Moore diagram of the state 11001010000 and then minimized the state table. Inside the state machine I gave 4-bit long variables to store my state as 11 bits were available and that can be stored in 4 bits. Used a basic switch case for determining the present and next state.

•Counter:

Now this 1 bit found was provided to the counter which also worked on the clock edge, if the found was high the bcd counter increased its count by 1 until it is either cleared by reset or max tick or crosses the value of 9999.


•Seven Segment Display:

We had to display the count on the seven-segment display of thebasys-3 board. Using the provide code for displaying hex from Lab G. The only thing that had to be taken care of was that the clock provide must be the boards one as we need high speed to execute the multiplexing on the board.


While Designing the Finite State Machine the overlapping is considered.

LFSR:

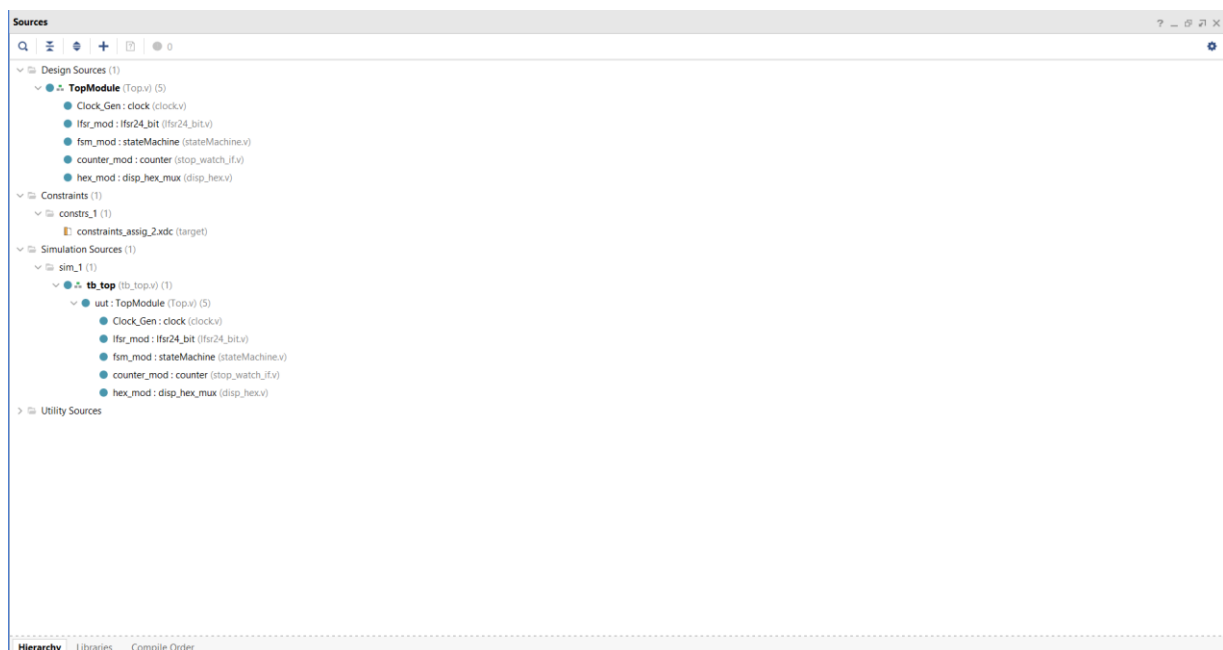
The seed value is given according to which the LFSR code is written and the tap values are taken from the XILINUX table. We should get the seed value when the reset is high in LFSR.




Hierarchy

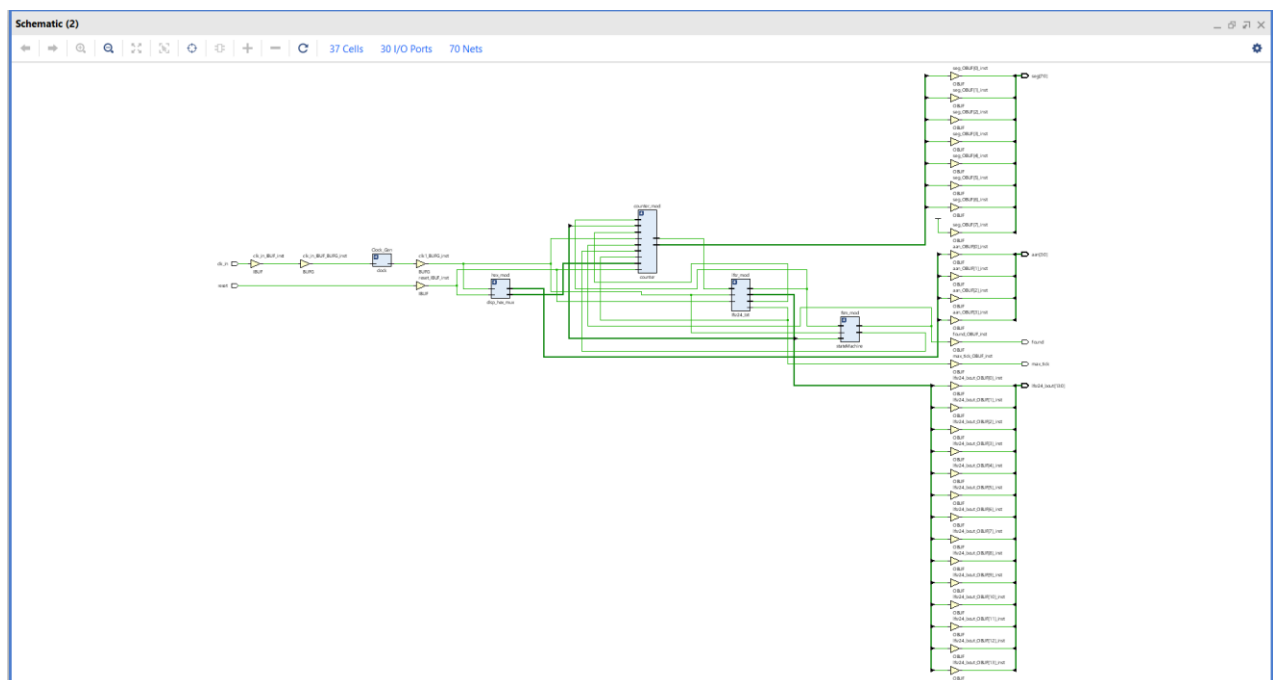
SCHEMATIC DIAGRAM:**TESTBENCH:**

Reset is set to high

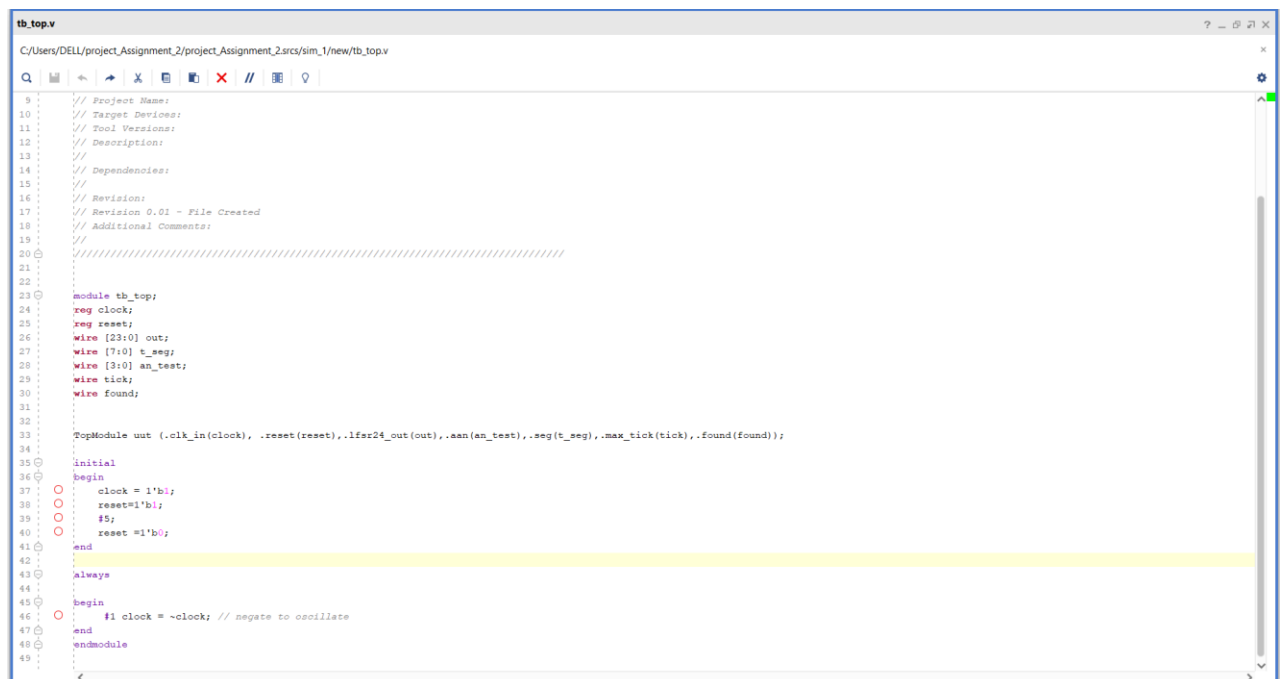

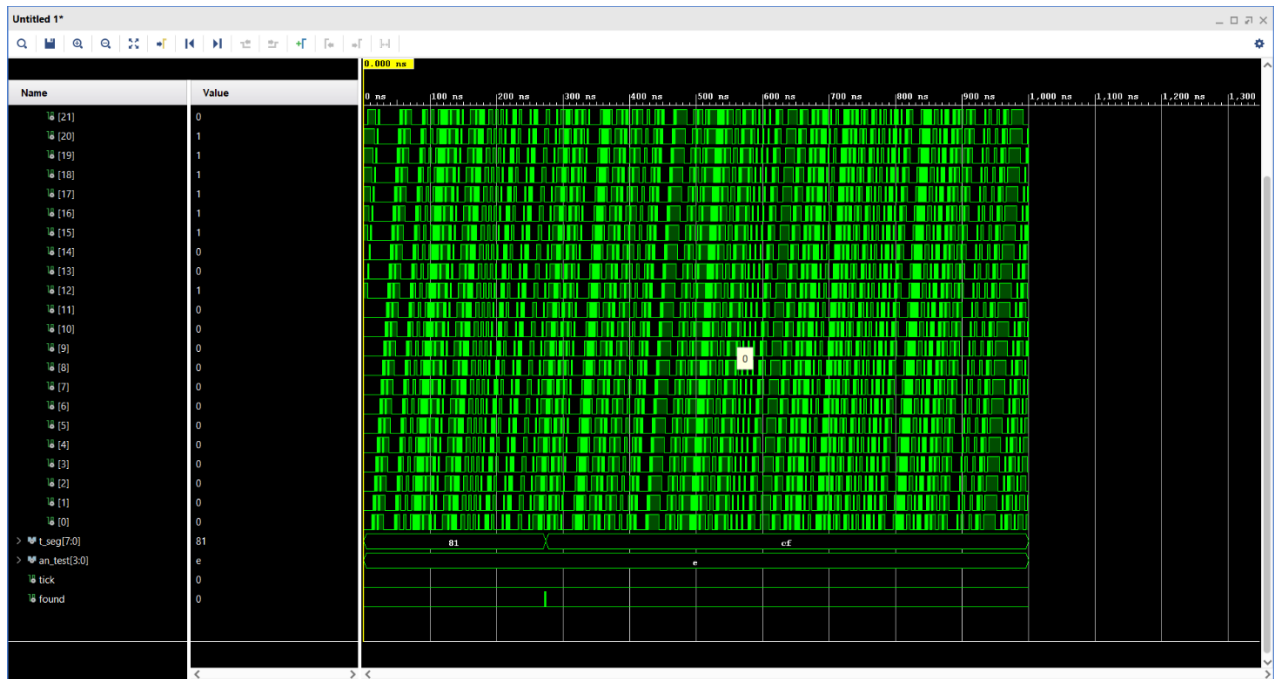When we use this testbench the output is:



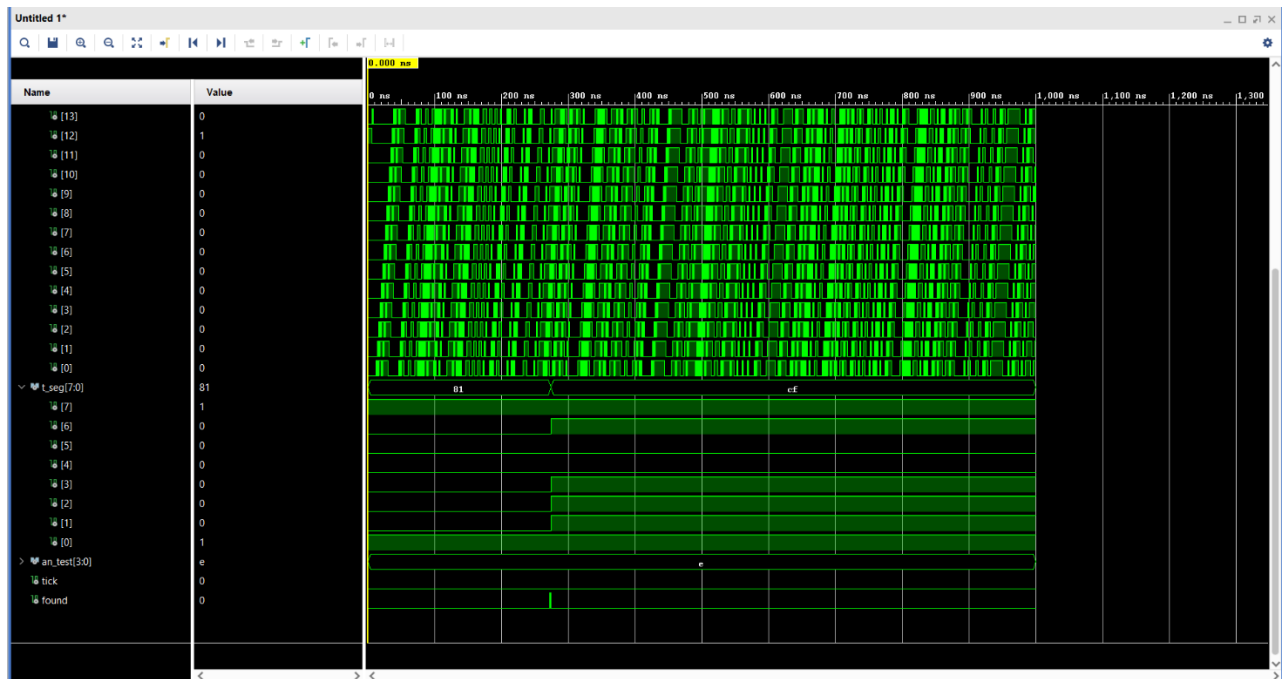

We can see whenever the found is high, on the next positive clock edge the counter increase the count.

FINDING THE PATTERN ACCORDING TO MOORE:

As there are 11 bits we take 12 bits to make the state diagram. Among which state A and L are same so it gets minimised.


Current State	Next State		Output	
	Input 0	Input 1	Input 0	Input 1
A	A	B	0	0
B	A	C	0	0
C	D	C	0	0
D	E	B	0	0
E	A	F	0	0
F	G	A	0	0
G	A	H	0	0
H	I	C	0	0
I	J	B	0	0
J	K	B	0	0
K	L	B	1	0

B	B,C									
C	A,D B,C	A,D								
D	A,E	A,E C,B	D,E C,B							
E	B,F	C,F	A,D C,F	A,E B,F						
F	A,G A,B	A,G A,C	D,G A,C	E,G A,B	A,G A,F					
G	B,H	A,H	A,D C,H	A,E B,H	F,H	A,G A,H				
H	A,I B,C	A,I	D,I	E,I B,C	A,I C,F	G,I A,C	A,I C,H			
I	A,J	A,J C,B	D,J C,B	E,J	A,J B,F	G,J A,B	A,G H,B	I,J C,B		
J	A,K	A,K C,B	D,K C,B	E,K	A,K B,F	G,K A,B	A,K B,H	I,K C,B	J,K	
K	A,L	A,L C,B	D,L C,B	E,L	A,L B,F	G,L A,B	A,L B,H	I,L C,B	J,L	K,L
L	✓	C,B	D,B C,B	A,E	F,B	A,G A,B	H,B	I,B C,B	A,J	A,K
	A	B	C	D	E	F	G	H	I	J


B	B,C									
C	A,D B,C	A,D								
D	A,E	A,E C,B	D,E C,B							
E	B,F	C,F	A,D C,F	A,E B,F						
F	A,G A,B	A,G A,C	D,G A,C	E,G A,B	A,G A,F					
G	B,H	A,H	A,D C,H	A,E B,H	F,H	A,G A,H				
H	A,I B,C	A,I	D,I	E,I B,C	A,I C,F	G,I A,C	A,I C,H			
I	A,J	A,J C,B	D,J C,B	E,J	A,J B,F	G,J A,B	A,G H,B	I,J C,B		
J	A,K	A,K C,B	D,K C,B	E,K	A,K B,F	G,K A,B	A,K B,H	I,K C,B	J,K	
K	A,L	A,L C,B	D,L C,B	E,L	A,L B,F	G,L A,B	A,L B,H	I,L C,B	J,L	K,L
L	✓	C,B	D,B C,B	A,E	F,B	A,G A,B	H,B	I,B C,B	A,J	A,K
	A	B	C	D	E	F	G	H	I	J

MINIMISING TABLE


FINITE STATE DIAGRAM

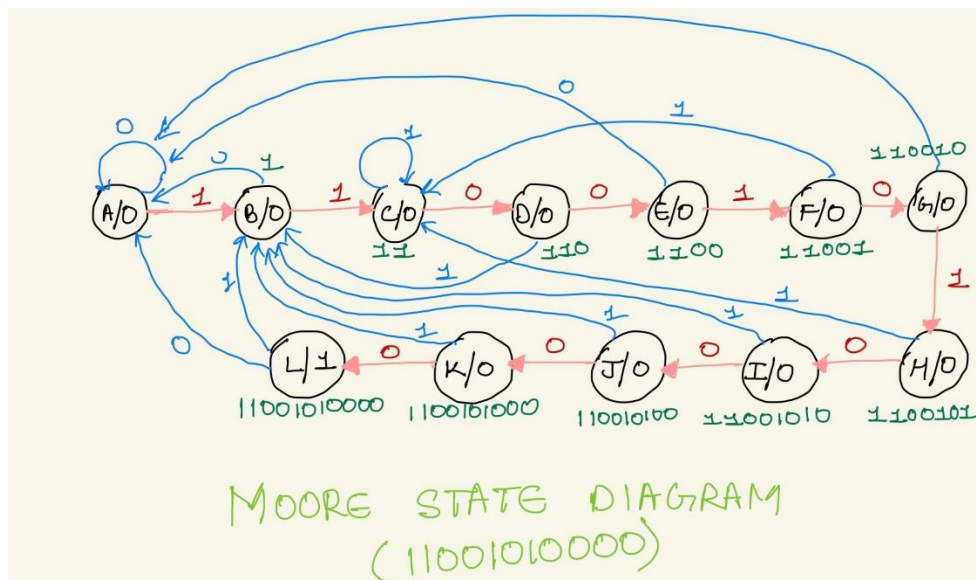

MINIMIZED STATE DIAGRAM:

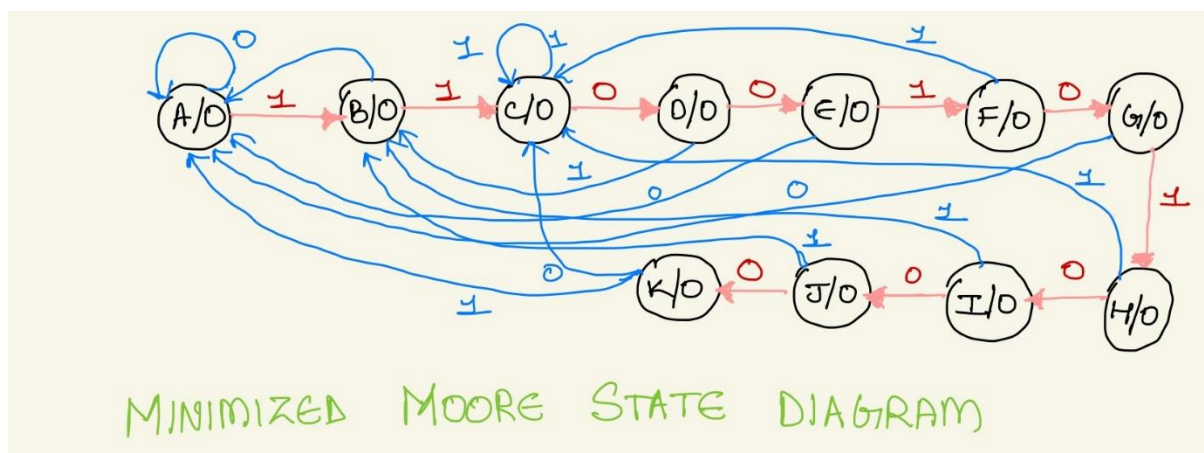


UTILIZATION REPORT:

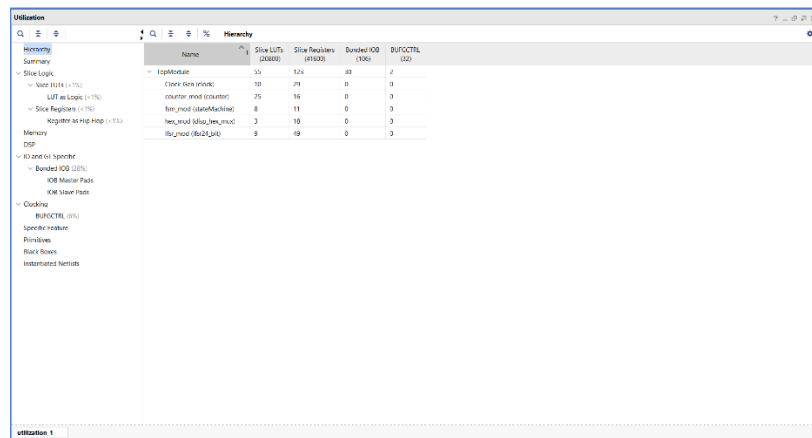


Hierarchy	Name	Slice LUTs (00000)	Slice Registers (01000)	Bonded IOB (100)	BUFGCTRL (10)
Summary					
▼ Slice Logic		55	124	89	2
▼ Slice LUTs (<1%)					
▼ LUT as Logic (<1%)					
▼ Slice Registers (<1%)					
▼ Register as Flip Flop (<1%)					
Memory					
DSP					
▼ IO and GT Specific					
▼ Bonded IOB (28%)					
IOB Master Pads					
IOB Slave Pads					
▼ Clocking					
BUFGCTRL (6%)					
Specific Feature					
Primitives					
Black Boxes					
Instantiated Netlists					

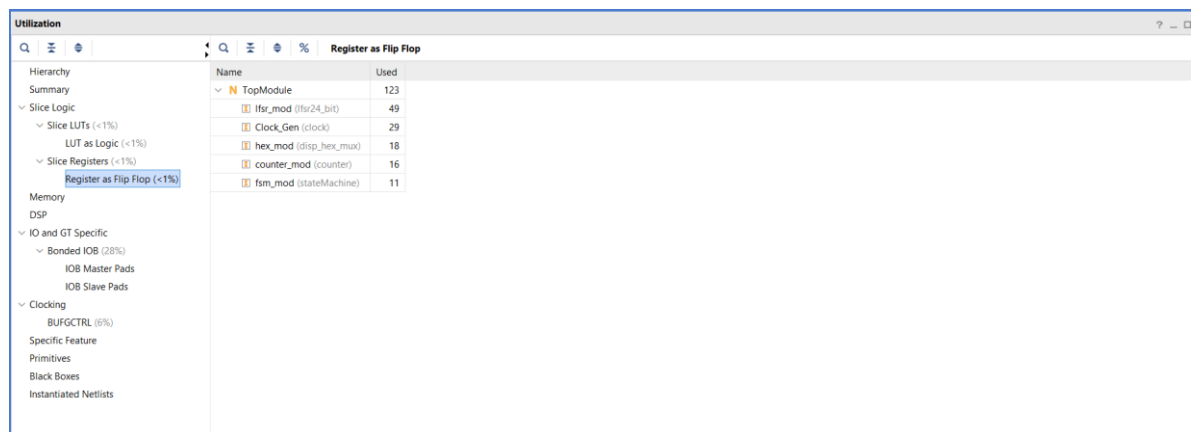UTILIZATION REPORT ACCORDING TO REGISTER FLIP FLOPS:





Hierarchy	Name	Used
Summary		
▼ Slice Logic		
▼ Slice LUTs (<1%)		
▼ LUT as Logic (<1%)		
▼ Slice Registers (<1%)		
▼ Register as Flip Flop (<1%)		
Memory		
DSP		
▼ IO and GT Specific		
▼ Bonded IOB (28%)		
IOB Master Pads		
IOB Slave Pads		
▼ Clocking		
BUFGCTRL (6%)		
Specific Feature		
Primitives		
Black Boxes		
Instantiated Netlists		

TIMING REPORT:

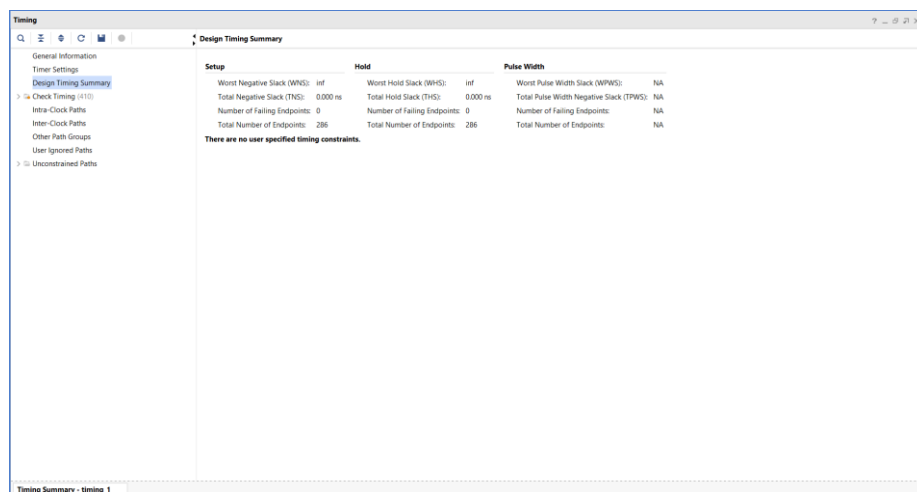

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): inf	Worst Hold Slack (WHS): inf	Worst Pulse Width Slack (WPWS): NA
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): NA
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: NA
Total Number of Endpoints: 286	Total Number of Endpoints: 286	Total Number of Endpoints: NA

There are no user specified timing constraints.

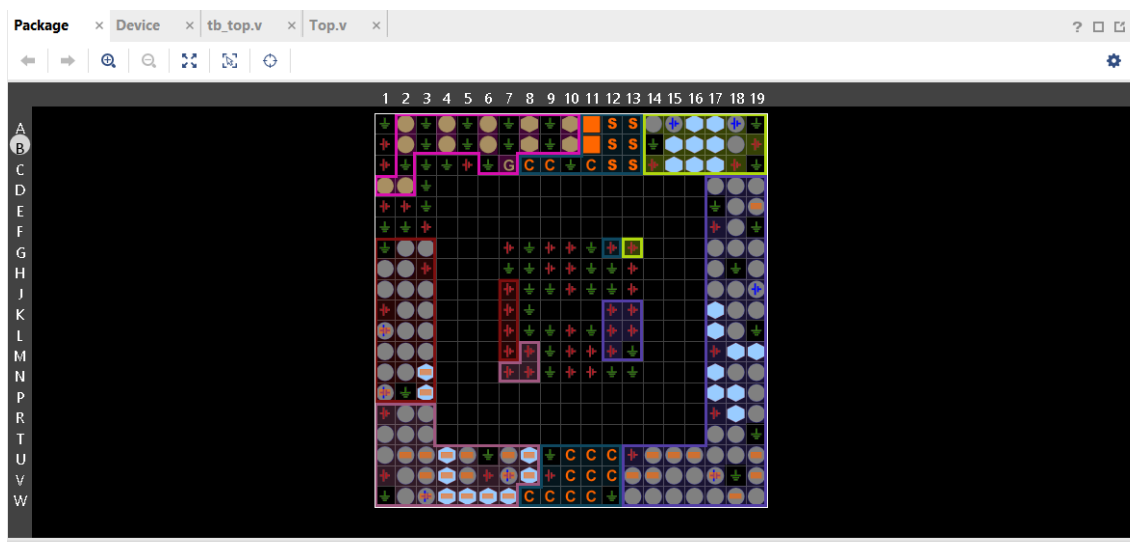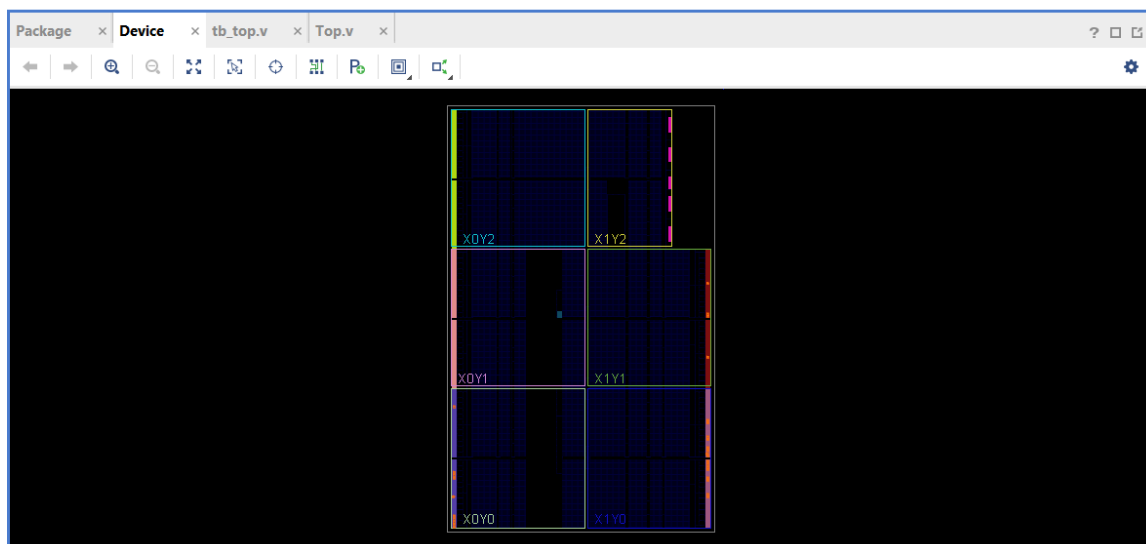PACKAGE:**DEVICE:**

1)CLOCK.V

2)LFSR24_BIT.V

3) COUNTER.V

```
stop_watch.v
```

```
1 // Listing 4.18
2 module counter
3 (
4     input wire clk,
5     input wire ps, clr,
6     output wire [3:0] d3,d2, d1, d0
7 );
8
9 // declaration
10 localparam DSIZE = 10000000;
11 reg [3:0] ma_reg;
12 wire [23:0] ma_next;
13 reg [3:0] d3_reg,d2_reg, d1_reg, d0_reg;
14 reg [3:0] d3_next,d2_next, d1_next, d0_next;
15 wire ma_tick;
16
17 // body
18 // register
19 always @(posedge clk)
20 begin
21     ma_reg <= ma_next;
22     d3_reg <= d3_next;
23     d2_reg <= d2_next;
24     d1_reg <= d1_next;
25     d0_reg <= d0_next;
26 end
27
28 // next-state logic
29 // 3.1 new tick generator: mod-8000000
30 assign ma_next = (clk && (ma_reg==DSIZE-4) go) ? 4'b0 :
31                 (go) ? ma_reg + 1 :
32                 ma_reg;
33 assign ma_tick = (ma_reg==DSIZE) ? 1'b1 : 1'b0;
34 // 3.2 tick and counter
35 always @*
36 begin
37     // default: keep the previous value
38     d0_next = d0_reg;
39     d1_next = d1_reg;
40     d2_next = d2_reg;
41     d3_next = d3_reg;
42 end
```

```

Step watch #1x
C:\Users\GOLL\project_Assigner_2\project_Assigner_2\source\1\reports\Provided stopwatch codepath watch_1x\
Q 1 2 3 1031 1
```

```

disp_hex.v
C:\Users\DELL\project_Assignment_2\srcs\source_1\hew\disp_hex.v

1 // timescale line | ipse
2 module disp_hex_mux
3 (
4     input wire clk, reset,
5     input wire [3:0] hex0, hex2, hex1, hex0, // hex digits
6     input wire [3:0] dp_in, // 4 decimal points
7     output reg [7:0] an, // enable 2-out-of-4 asserted low
8     output reg [7:0] cseg // 2nd segments
9 );
10 // constant declaration
11 // refreshing rate around 800 Hz (50 MHz/2^16)
12 localparam M = 18;
13 // internal signal declaration
14 reg [M-1:0] q_seg;
15 wire [M-1:0] q_next;
16 reg [3:0] hex_in;
17 reg dp;
18 // 8-bit counter
19 // register
20 always @(posedge clk)
21 if (reset)
22     q_seg <= 0;
23 else
24     q_seg <= q_next;
25 // next-state logic
26 assign q_next = q_seg + 1;
27 // 2 MHz of counter to control 4-to-1 multiplexing
28 // and to generate active-low enable signal
29 always #*
30 case (q_seg[M-1:M-2])
31     2'b01:
32         begin
33             an = 4'b1100;
34             hex_in = hex0;
35             dp = dp_in[0];
36         end
37     2'b01:
38         begin
39             an = 4'b1010;
40             hex_in = hex1;
41             dp = dp_in[1];
42         end
43     // ...
44 endcase

```

```

disp_hex.v
C:/Users/DELL/project_Assignment_2/project_Assignment_2/srcs/sources_1/new/disp_hex.v

37: 2'b01;
38: begin
39:   an = 4'b1001;
40:   hex_in = hex1;
41:   dp = dp_in[1];
42: end
43: 2'b01;
44: begin
45:   an = 4'b0111;
46:   hex_in = hex2;
47:   dp = dp_in[2];
48: end
49: 2'b11;
50: begin
51:   an = 4'b0111;
52:   hex_in = hex3;
53:   dp = dp_in[3];
54: end
55: default:
56:   begin
57:     an = 4'b0111;
58:     hex_in = hex3;
59:     dp = dp_in[3];
60:   end
61: endcase
62: // hex to seven-segment led display
63:
64: always @*
65: begin
66:   case(hex_in)
67:     4'h1: seg[6:0] = 7'b0000001;
68:     4'h1: seg[6:0] = 7'b0001111;
69:     4'h1: seg[6:0] = 7'b0000011;
70:     4'h1: seg[6:0] = 7'b0000111;
71:     4'h1: seg[6:0] = 7'b0011001;
72:     4'h1: seg[6:0] = 7'b0100101;
73:     4'h1: seg[6:0] = 7'b0100001;
74:     4'h1: seg[6:0] = 7'b0011111;
75:     4'h1: seg[6:0] = 7'b0000001;
76:     4'h1: seg[6:0] = 7'b0000101;
77:     4'h1: seg[6:0] = 7'b0001001;
78:   end
79:   endcase
80:   // an = seg[6:0]
81:   end

```

```

disp_hex.v
C:/Users/DELL/project_Assignment_2/project_Assignment_2/srcs/sources_1/new/disp_hex.v

49: end
50: 2'b11;
51: begin
52:   an = 4'b0111;
53:   hex_in = hex3;
54:   dp = dp_in[3];
55: end
56: default:
57:   begin
58:     an = 4'b0111;
59:     hex_in = hex3;
60:     dp = dp_in[3];
61:   end
62: endcase
63: // hex to seven-segment led display
64:
65: always @*
66: begin
67:   case(hex_in)
68:     4'h1: seg[6:0] = 7'b0000001;
69:     4'h1: seg[6:0] = 7'b0001111;
70:     4'h1: seg[6:0] = 7'b0000011;
71:     4'h1: seg[6:0] = 7'b0000111;
72:     4'h1: seg[6:0] = 7'b0011001;
73:     4'h1: seg[6:0] = 7'b0100101;
74:     4'h1: seg[6:0] = 7'b0100001;
75:     4'h1: seg[6:0] = 7'b0011111;
76:     4'h1: seg[6:0] = 7'b0000001;
77:     4'h1: seg[6:0] = 7'b0000101;
78:     4'h1: seg[6:0] = 7'b0001001;
79:     4'h1: seg[6:0] = 7'b0000011;
80:     4'h1: seg[6:0] = 7'b0000111;
81:     4'h1: seg[6:0] = 7'b0011001;
82:   end
83:   default:
84:     seg[6:0] = 7'b0111001;
85:   endcase
86:   seg[7] = dp;
87: end
88: endmodule
89:

```

5) STATE MACHINE

```

stateMachine.v
C:/Users/DELL/project_Assignment_2/project_Assignment_2/srcs/sources_1/new/stateMachine.v

1: timescale 1ns / 1ps
2: timescale 1ns / 1ps
3: module stateMachine
4: (
5:   input wire clk, reset,
6:   input wire seg,
7:   output reg tick
8: );
9: // symbolic state declaration
10: localparam A = 4'b0001;
11: A = 4'b0001;
12: D = 4'b0011;
13: D = 4'b0011;
14: E = 4'b0101;
15: F = 4'b0101;
16: G = 4'b0110;
17: H = 4'b0111;
18: I = 4'b1000;
19: J = 4'b1001;
20: K = 4'b1001;
21:
22: reg [3:0] state_reg, state_next;
23:
24: always @(posedge clk, posedge reset)
25: begin
26:   if (reset)
27:     state_reg <= A;
28:   else
29:     state_reg <= state_next;
30: end
31: // next-state logic and output logic
32: always @*
33: begin
34:   state_next = state_reg;
35:   // default: state is same
36:   tick = 1'b0; // default: outputs: 0
37:   case (state_reg)
38:     A:
39:       if (seg)
40:         state_next = H;
41:       else
42:         state_next = A;
43:   end
44: end

```

```
stateMachine.v
C:/Users/DELL/project_Assignment_2/project_Assignment_2/srcs/sources_1/new/stateMachine.v

37:0 case (state_reg)
38:0 A:
39:0 if (enq)
40:0 state_next = B;
41:0 else
42:0 state_next = A;
43:0 B:
44:0 if (enq)
45:0 state_next = C;
46:0 else
47:0 state_next = A;
48:0 C:
49:0 if (~enq)
50:0 state_next = D;
51:0 else
52:0 state_next = C;
53:0 D:
54:0 if (~enq)
55:0 state_next = E;
56:0 else
57:0 state_next = B;
58:0 E:
59:0 if (enq)
60:0 state_next = F;
61:0 else
62:0 state_next = C;
63:0 F:
64:0 if (~enq)
65:0 state_next = D;
66:0 else
67:0 state_next = A;
68:0 G:
69:0 if (enq)
70:0 state_next = H;
71:0 else
72:0 state_next = C;
73:0 H:
74:0 if (~enq)
75:0 state_next = I;
76:0 else
77:0 state_next = B;
```

```
stateMachine.v
C:/Users/DELL/project_Assignment_2/project_Assignment_2/srcs/sources_1/new/stateMachine.v

68:0 state_next = G;
69:0 else
70:0 state_next = A;
71:0 G:
72:0 if (enq)
73:0 state_next = B;
74:0 else
75:0 state_next = C;
76:0 H:
77:0 if (~enq)
78:0 state_next = D;
79:0 else
80:0 state_next = J;
81:0 J:
82:0 if (~enq)
83:0 state_next = K;
84:0 else
85:0 state_next = B;
86:0 K:
87:0 if (~enq)
88:0 begin
89:0 state_next = A;
90:0 lock1'b1;
91:0 end
92:0 else
93:0 state_next = B;
94:0 L:
95:0 default:
96:0 begin
97:0 state_next = A;
98:0 lock1'b1;
99:0 end
100:0 endcase
101:0 end
102:0 endmodule
103:0 endmodule
104:0 endmodule
105:0
```

CONSTRAINTS (XDC FILE)

```
constraints_assig.2.xdc
C:/Users/DELL/project_Assignment_2/project_Assignment_2/srcs/constrs_1/new/constraints_assig.2.xdc

1: set_property TOPSTANDARD LVCMOS33 [get_ports {aen[0]}]
2: set_property TOPSTANDARD LVCMOS33 [get_ports {aen[1]}]
3: set_property TOPSTANDARD LVCMOS33 [get_ports {aen[1]}]
4: set_property TOPSTANDARD LVCMOS33 [get_ports {aen[0]}]
5: set_property TOPSTANDARD LVCMOS33 [get_ports {ifaz24_bout[13]}]
6: set_property TOPSTANDARD LVCMOS33 [get_ports {ifaz24_bout[12]}]
7: set_property TOPSTANDARD LVCMOS33 [get_ports {ifaz24_bout[11]}]
8: set_property TOPSTANDARD LVCMOS33 [get_ports {ifaz24_bout[10]}]
9: set_property TOPSTANDARD LVCMOS33 [get_ports {ifaz24_bout[9]}]
10: set_property TOPSTANDARD LVCMOS33 [get_ports {ifaz24_bout[8]}]
11: set_property TOPSTANDARD LVCMOS33 [get_ports {ifaz24_bout[7]}]
12: set_property TOPSTANDARD LVCMOS33 [get_ports {ifaz24_bout[6]}]
13: set_property TOPSTANDARD LVCMOS33 [get_ports {ifaz24_bout[5]}]
14: set_property TOPSTANDARD LVCMOS33 [get_ports {ifaz24_bout[4]}]
15: set_property TOPSTANDARD LVCMOS33 [get_ports {ifaz24_bout[3]}]
16: set_property TOPSTANDARD LVCMOS33 [get_ports {ifaz24_bout[2]}]
17: set_property TOPSTANDARD LVCMOS33 [get_ports {ifaz24_bout[1]}]
18: set_property TOPSTANDARD LVCMOS33 [get_ports {ifaz24_bout[0]}]
19: set_property TOPSTANDARD LVCMOS33 [get_ports {enq[7]}]
20: set_property TOPSTANDARD LVCMOS33 [get_ports {enq[6]}]
21: set_property TOPSTANDARD LVCMOS33 [get_ports {enq[5]}]
22: set_property TOPSTANDARD LVCMOS33 [get_ports {enq[4]}]
23: set_property TOPSTANDARD LVCMOS33 [get_ports {enq[3]}]
24: set_property TOPSTANDARD LVCMOS33 [get_ports {enq[2]}]
25: set_property TOPSTANDARD LVCMOS33 [get_ports {enq[1]}]
26: set_property TOPSTANDARD LVCMOS33 [get_ports {enq[0]}]
27: set_property PACKAGE_PIN W4 [get_ports {aen[0]}]
28: set_property PACKAGE_PIN V4 [get_ports {aen[1]}]
29: set_property PACKAGE_PIN U4 [get_ports {aen[1]}]
30: set_property PACKAGE_PIN U2 [get_ports {aen[0]}]
31: set_property PACKAGE_PIN N3 [get_ports {ifaz24_bout[13]}]
32: set_property PACKAGE_PIN N3 [get_ports {ifaz24_bout[12]}]
33: set_property PACKAGE_PIN O3 [get_ports {ifaz24_bout[11]}]
34: set_property PACKAGE_PIN W3 [get_ports {ifaz24_bout[10]}]
35: set_property PACKAGE_PIN V3 [get_ports {ifaz24_bout[9]}]
36: set_property PACKAGE_PIN V13 [get_ports {ifaz24_bout[8]}]
37: set_property PACKAGE_PIN V14 [get_ports {ifaz24_bout[7]}]
38: set_property PACKAGE_PIN U14 [get_ports {ifaz24_bout[6]}]
39: set_property PACKAGE_PIN U15 [get_ports {ifaz24_bout[5]}]
40: set_property PACKAGE_PIN W18 [get_ports {ifaz24_bout[4]}]
41: set_property PACKAGE_PIN V19 [get_ports {ifaz24_bout[3]}]
```

```
constraints_assign_2.xdc
C:\Users\DELL\project_Assignment_2\srcs\constr_1\new\constraints_assign_2.xdc

set_property IOSTANDARD LVCMOS33 [get_ports {seg[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[10]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[0]}]
set_property PACKAGE_PIN W4 [get_ports {aan[3]}]
set_property PACKAGE_PIN V4 [get_ports {aan[2]}]
set_property PACKAGE_PIN U4 [get_ports {aan[1]}]
set_property PACKAGE_PIN U2 [get_ports {aan[0]}]
set_property PACKAGE_PIN N3 [get_ports {ifw24_bout[13]}]
set_property PACKAGE_PIN P3 [get_ports {ifw24_bout[12]}]
set_property PACKAGE_PIN U3 [get_ports {ifw24_bout[11]}]
set_property PACKAGE_PIN W3 [get_ports {ifw24_bout[10]}]
set_property PACKAGE_PIN V3 [get_ports {ifw24_bout[9]}]
set_property PACKAGE_PIN U15 [get_ports {ifw24_bout[5]}]
set_property PACKAGE_PIN V14 [get_ports {ifw24_bout[7]}]
set_property PACKAGE_PIN U14 [get_ports {ifw24_bout[6]}]
set_property PACKAGE_PIN U15 [get_ports {ifw24_bout[5]}]
set_property PACKAGE_PIN W10 [get_ports {ifw24_bout[4]}]
set_property PACKAGE_PIN V19 [get_ports {ifw24_bout[3]}]
set_property PACKAGE_PIN U19 [get_ports {ifw24_bout[2]}]
set_property PACKAGE_PIN K19 [get_ports {ifw24_bout[1]}]
set_property PACKAGE_PIN U16 [get_ports {ifw24_bout[0]}]
set_property PACKAGE_PIN V7 [get_ports {seg[7]}]
set_property PACKAGE_PIN W7 [get_ports {seg[6]}]
set_property PACKAGE_PIN W6 [get_ports {seg[5]}]
set_property PACKAGE_PIN U8 [get_ports {seg[4]}]
set_property PACKAGE_PIN V8 [get_ports {seg[3]}]
set_property PACKAGE_PIN U5 [get_ports {seg[2]}]
set_property PACKAGE_PIN V5 [get_ports {seg[1]}]
set_property PACKAGE_PIN U7 [get_ports {seg[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports clk_in]
set_property PACKAGE_PIN W5 [get_ports clk_in]
set_property PACKAGE_PIN V17 [get_ports reset]
set_property IOSTANDARD LVCMOS33 [get_ports reset]

set_property IOSTANDARD LVCMOS33 [get_ports found]
set_property IOSTANDARD LVCMOS33 [get_ports max_tick]
set_property PACKAGE_PIN P1 [get_ports max_tick]
set_property PACKAGE_PIN L1 [get_ports found]
```

I/O Ports

Name	Direction	Board Part Pin	Board Part Interface	Neg Diff Pair	Package Pin	Fixed	Bank	I/O Std	Vcco	Vref	Drive Strength	Slew Type	Pull Type	Off-Chip Te
▼ All ports (30)														
▼ aan (4)						<input checked="" type="checkbox"/>								
aan[3]	OUT				W4	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
aan[2]	OUT				V4	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
aan[1]	OUT				U4	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
aan[0]	OUT				U2	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
▼ ifw24_bout (14)						<input checked="" type="checkbox"/>	(Multiple)	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
ifw24_bout...	OUT				N3	<input checked="" type="checkbox"/>	35	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
ifw24_bout...	OUT				P3	<input checked="" type="checkbox"/>	35	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
ifw24_bout...	OUT				U3	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
ifw24_bout...	OUT				W3	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
ifw24_bout...	OUT				V3	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
ifw24_bout...	OUT				V13	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
ifw24_bout...	OUT				V14	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
ifw24_bout...	OUT				U14	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
ifw24_bout...	OUT				U15	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
ifw24_bout...	OUT				W18	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
ifw24_bout...	OUT				V19	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
ifw24_bout...	OUT				U19	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
ifw24_bout...	OUT				E19	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
ifw24_bout...	OUT				U16	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
▼ seg (8)						<input checked="" type="checkbox"/>								
seg[7]	OUT				V7	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
seg[6]	OUT				W7	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
seg[5]	OUT				W6	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
seg[4]	OUT				U8	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
seg[3]	OUT				V8	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
seg[2]	OUT				U5	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
seg[1]	OUT				V5	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50
seg[0]	OUT				U7	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	▼ SLOW	▼ NONE	▼	FP_VTT_50


End of page (1)

I/O Ports															?		?		?	
Name	Direction	Board Part Pin	Board Part Interface	Neg Diff Pair	Package Pin	Fixed	Bank	I/O Std	V _{CCO}	V _{ref}	Drive Strength	Slew Type	Pull Type	Off-Chip Termination						
▼ seg [0]																				
aan[0]	OUT				U2	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
▼ ifw24_bout [14]																				
ifw24_bout[14]	OUT					<input checked="" type="checkbox"/>	(Multiple)	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
ifw24_bout[13]	OUT				N3	<input checked="" type="checkbox"/>	35	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
ifw24_bout[12]	OUT				P3	<input checked="" type="checkbox"/>	35	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
ifw24_bout[11]	OUT				U3	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
ifw24_bout[10]	OUT				W3	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
ifw24_bout[9]	OUT				V3	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
ifw24_bout[8]	OUT				V13	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
ifw24_bout[7]	OUT				V14	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
ifw24_bout[6]	OUT				U14	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
ifw24_bout[5]	OUT				U15	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
ifw24_bout[4]	OUT				W18	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
ifw24_bout[3]	OUT				V19	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
ifw24_bout[2]	OUT				U19	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
ifw24_bout[1]	OUT				E19	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
ifw24_bout[0]	OUT				U16	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
▼ seg [1]																				
seg[7]	OUT				V7	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
seg[6]	OUT				W7	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
seg[5]	OUT				W6	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
seg[4]	OUT				U8	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
seg[3]	OUT				V8	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
seg[2]	OUT				U5	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
seg[1]	OUT				V5	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
seg[0]	OUT				U7	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
▼ Scalar ports [4]																				
clk_in	IN				W5	<input checked="" type="checkbox"/>	34	LVCMOS33*	3.300			NONE	NONE							
found	OUT				L1	<input checked="" type="checkbox"/>	35	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
max_tick	OUT				P1	<input checked="" type="checkbox"/>	35	LVCMOS33*	3.300	12	SLOW	NONE	NONE	FP_VTT_50						
reset	IN				V17	<input checked="" type="checkbox"/>	14	LVCMOS33*	3.300			NONE	NONE							

DEMO:

Now when we generate the bitstream and the reset is high so the output on the board is as follows:



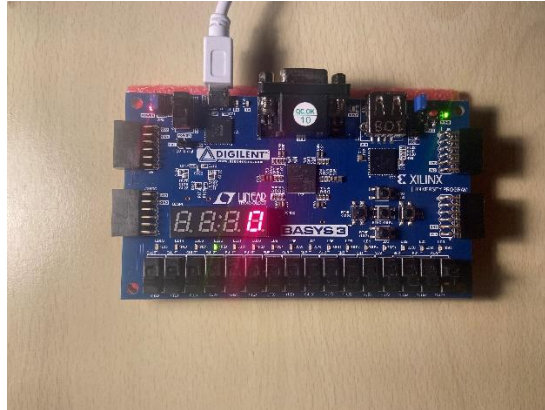
My seed value is 100111111001000000000000. I define the LFSR for 14 bits and output the seed value now comes from the left 14 bits. So now the 1 led lights up.



When we generate the full bitstream. The counter goes on and lfsr bits are also shown. The video link is attached for DEMO.

As soon as we run the bit file the led's start to blink with the speed initialised in the clock.v file.

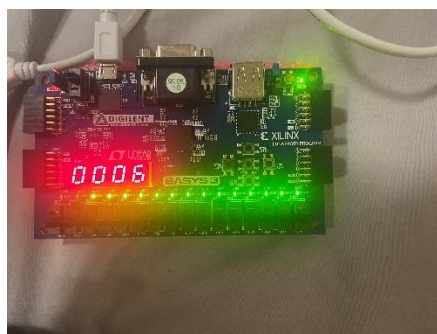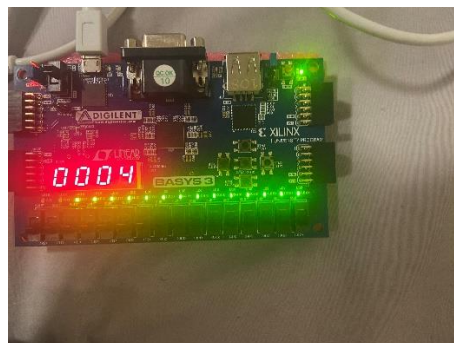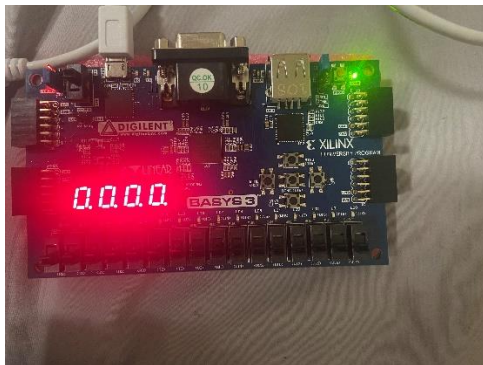The counter starts from 0 and goes on till 9999 on the BASYS 3 board. My LFSR cycle goes on till $2^{24}-1$. While the seven segment decoder goes on the speed of the clock is too high so the blinking of the LED's can't be seen.



The demo video is in the link below.

In the DEMO video as the max_tick becomes 1 the counter increases.

LINK: https://drive.google.com/file/d/195bqEcnWrSvQPf0e_AKP8e8wh1fiKTaG/view?usp=sharing

The clock in this project is being handled by the CLK_IN in the xdc file.

The output of the counter is the number of times the same pattern is getting generated.

-SHRUTI KATHURIA

